

## Integrated Systems Architectures

### Lab 1: design and implementation of a digital filter Assignment

Read the Lab 1 description and address the following points.

#### 1 Reference model development

- (a) Design the filter with Matlab/Octave and represent the coefficients with the number of bits which have been assigned to your group. Put in the report a figure showing the frequency response for both floating point and fixed point coefficients. Comment it.
- (b) Develop the fixed point model as a C program and reduce the precision of the multiplications reaching a maximum THD of -30 dB.
- (c) Compare and comment the results.

#### 2 VLSI implementation

- Develop the architecture of the filter (direct-form for FIR filters and direct-form-II/canonical-direct-form for IIR filters) by placing the proper number of registers, adders, multipliers and logic. Draw the timing diagram of the architecture showing it is compliant with the specifications (use <https://wavedrom.com> for the timing diagram).
- Develop the VHDL model of the filter and verify it against the fixed point C model with a proper testbench.  
The results given by the VHDL model must be equal to the ones obtained with the C model.  
Show that the results of the VHDL model are correct (equal to the results of the C model) even when VIN moves from '1' to '0' and then back to '1'.  
Be sure that the interface of your architecture is exactly

equal to the one shown in *es1v3.0\_description.pdf* as an automatic tool will be used to check your design.

- Measure the amount of time required to complete the simulation (from the first rising edge of the clock sampling VOUT='1' to the last rising edge of the clock sampling VOUT='1').
- Perform the logic synthesis and find the maximum clock frequency at which the design can correctly run (minimum period giving slack *met* and equal to zero). Then, find the area.
- Set  $f_{clk} = f_M/4$ , find the area, verify the design, measure the amount of time required to complete the simulation and estimate the power consumption.
- Place & Route the design at  $f_{clk} = f_M/4$ , find the area, verify the design, measure the amount of time required to complete the simulation and estimate the power consumption.

### **3 Advanced architecture development**

- Develop a new C model to take into account the modifications required by the advanced architecture.
- Verify that the THD requirement is still satisfied.
- Change the interface of your filter according with the description given in *es1v3.0\_description.pdf*.
- Repeat all the steps in 2.